

MULTIMEDIA



UNIVERSITY

STUDENT ID NO

--	--	--	--	--	--	--	--	--	--

MULTIMEDIA UNIVERSITY

FINAL EXAMINATION

TRIMESTER 2, 2016/2017

**EEE2146 – MICROELECTRONIC CIRCUIT  
ANALYSIS AND DESIGN**

( All sections / Groups )

4 MARCH 2017  
9.00 a.m – 11.00 a.m  
( 2 Hours )


---

**INSTRUCTIONS TO STUDENTS**

1. This examination paper consists of 6 pages with 4 questions only.
2. Attempt **ALL FOUR** questions. All questions carry equal marks and the distribution of the marks for each question is given.
3. Please print all your answers in the Answer Booklet provided.

**Question 1**


- (a) Compute the transistor base current,  $I_B$ , emitter current,  $I_E$ , emitter voltage,  $V_E$  and base voltage,  $V_B$  (with respect to ground) of the circuit shown in Figure Q1. Given that  $V_{CC} = 9\text{ V}$  and the transistor  $V_{BE(\text{active})} = 0.7\text{ V}$ , current gain  $\beta = 100$  and early voltage  $V_A = \infty$ . [7 marks]
- (b) Draw the small-signal equivalent circuit of the amplifier circuit in Figure Q1 using the simplified hybrid model. [5 marks]
- (c) From the small-signal equivalent circuit, determine the small signal input resistance,  $R_{IN}$  and the overall voltage gain,  $\frac{V_o}{V_s}$ . Given that voltage equivalence of temperature  $V_T = 26\text{ mV}$ . [13 marks]

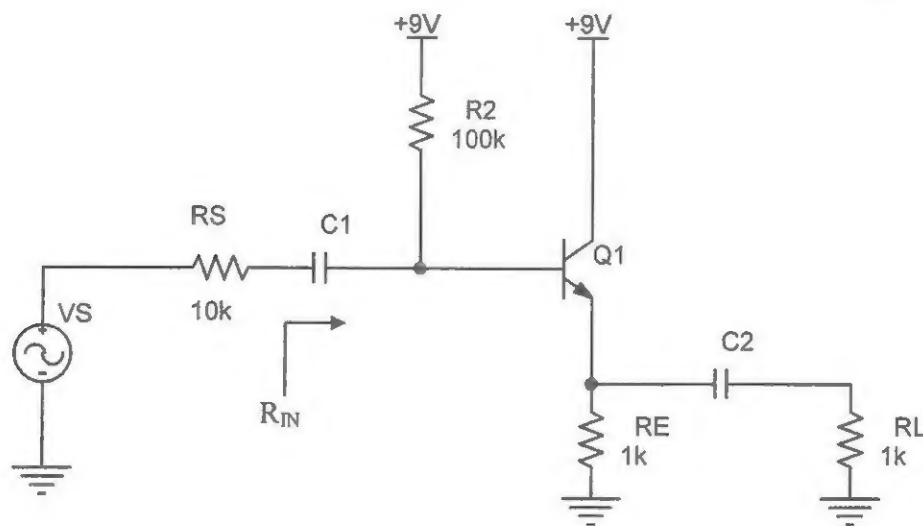**Figure Q1****Continued...**

**Question 2**

The circuit shown in Figure Q2 is a common-source amplifier. The transistor has  $V_t = 1.5\text{V}$ ,  $k'_n(W/L) = 0.25\text{ mA/V}^2$  and  $V_A = 50\text{ V}$ .

- (a) From the DC analysis, compute the values for DC drain current,  $I_D$  and DC drain voltage,  $V_D$ . Assume the DC gate current,  $I_G = 0$ . [7 marks]
- (b) Draw a small-signal equivalent circuit for the circuit shown in Figure Q2 using the simplified hybrid model. [5 marks]
- (c) Derive and compute the small-signal voltage gain,  $\frac{v_o}{v_i}$ , then compute the input resistance  $R_{IN}$ . [13 marks]

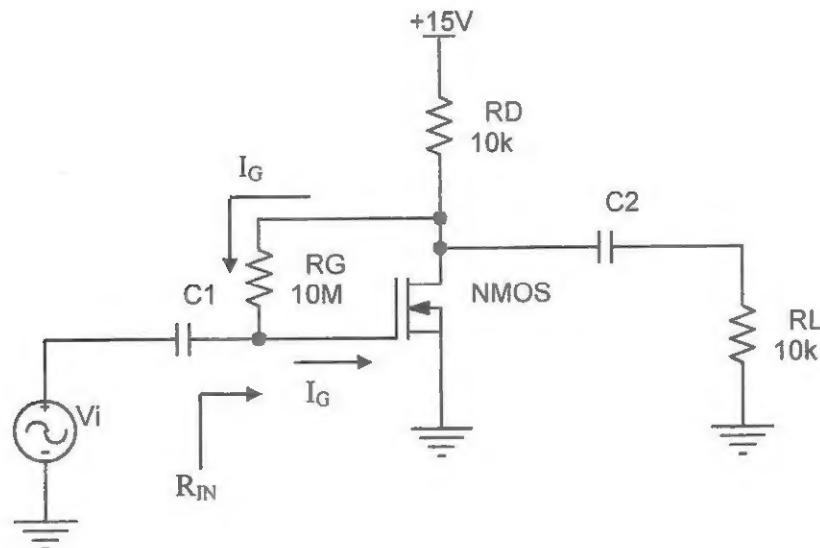

**Figure Q2**

**Question 3**


Figure Q3 below shows a MOSFET current mirror and a MOSFET differential amplifier. The voltage supply  $V_{DD} = V_{SS} = 1.5V$ . Assume that all transistors are identical (same  $k_n$  and  $V_t$ ) and the transistors are in saturation.

- (a) Find  $I_{REF}$  if  $V_{GS4} = V_{GS3} = 1V$  and  $R_1 = 2.5k\Omega$ . Then, compute  $I_q$  when  $(W/L)_4 = 2$ ,  $(W/L)_3 = 4$ ,  $k_n = 200\mu A/V^2$  and  $V_t = 0.5V$ . [6 marks]

- (b) Draw the differential-mode small signal equivalent circuit for the differential amplifier below, then prove that the differential-mode voltage gain,

$$A_d = \frac{V_{od}}{V_{id}} = -g_m (R_D \parallel r_o). \quad [9 \text{ marks}]$$

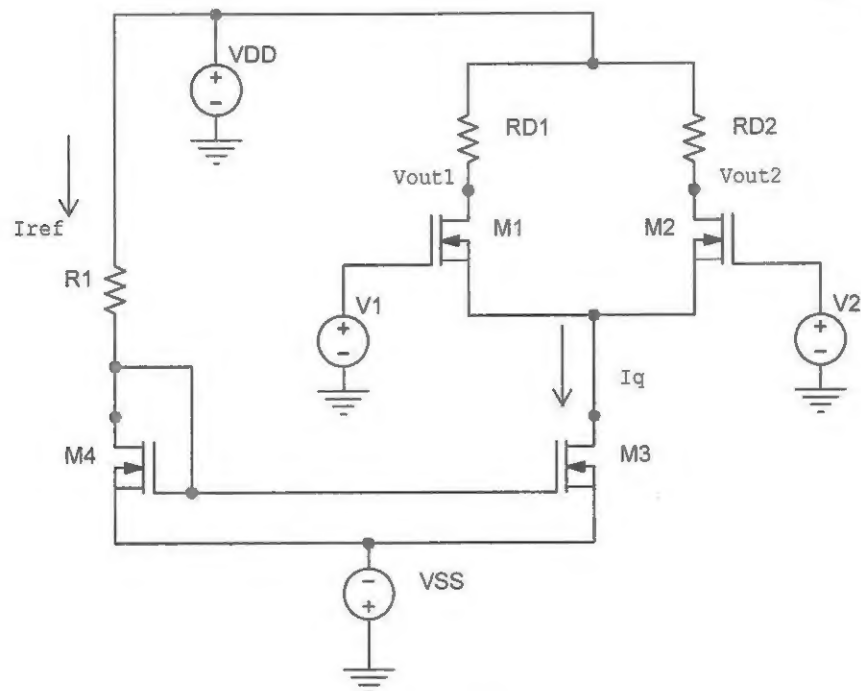- (c) Then, compute the values of  $R_{D1}$  and  $R_{D2}$ . Assume M1 and M2 are identical with  $V_{OV} = 0.5$ , early voltage,  $V_A = \infty$  and the differential-mode voltage gain,  $A_d = -250$ . [10 marks]

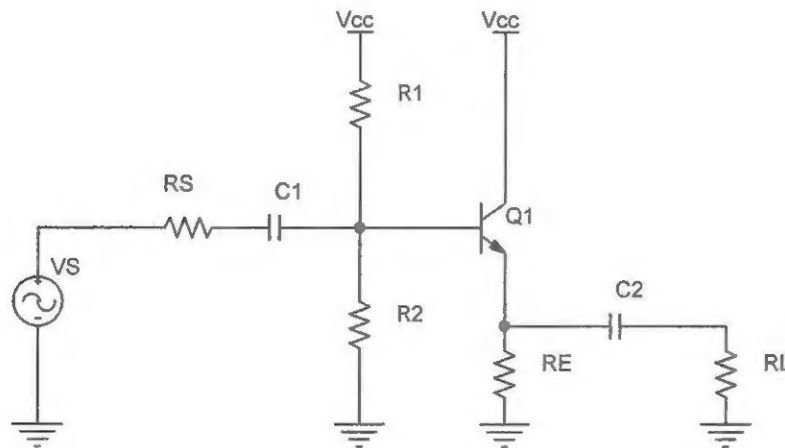


**Figure Q3**

**Question 4**


- (a) Draw a low frequency small signal equivalent circuit of the circuit shown in Figure Q4 (a) using hybrid- $\pi$  model. Ignore the effect of the transistor output resistance,  $r_o$ . Then, derive the equations for the lower cutoff frequencies  $f_{C1}$  and  $f_{C2}$  of the circuits. Use necessary equivalent circuits to show in your derivations.

[11 marks]

**Figure Q4(a)**

- (b) The non-inverting amplifier shown in Figure Q4 (b) is a series-series feedback transconductance amplifier. Derive the equations for gain  $A_f$ , output resistance  $R_{of}$  and input resistance  $R_{if}$ . Draw the amplifier equivalent circuit to assist the derivations.

[14 marks]

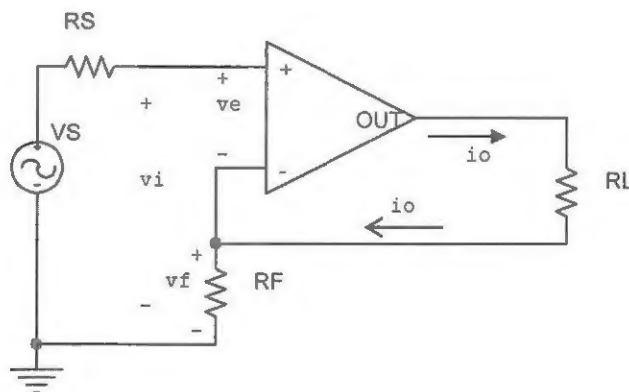**Figure Q4(b)**

Continued...

**Appendix: Useful formula**

$$V_T = \frac{kT}{q} \approx 26\text{mV}$$

$$I_B = \frac{I_C}{\beta_F}$$

$$I_E = \frac{-I_C}{\alpha_F}$$

$$I_C = I_S \left( \exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right) \left( 1 + \frac{V_{CE}}{V_A} \right)$$

$$g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{I_C}{V_T}$$

$$C_b = \tau_F g_m$$

$$r_\pi = \frac{\beta}{g_m} = \frac{\beta V_T}{I_C} = \frac{V_T}{I_B}$$

$$g_m v_\pi = \beta i_b$$

$$r_o = \frac{1}{\frac{\partial I_C}{\partial V_{CE}}} = \frac{V_A}{I_C}$$

$$r_\mu = \beta r_o$$

$$V_{DS} < V_{GS} - V_t;$$

$$I_D = k' \left( \frac{W}{L} \right) \left[ (V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$r_{ds} = \frac{V_{DS}}{i_D}$$

$$V_{DS} > V_{GS} - V_t;$$

$$I_D = \frac{k'}{2} \left( \frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$V_{DS} > V_{DS(\text{SAT})};$$

$$I_D = \frac{k'}{2} \left( \frac{W}{L} \right) (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

$$V_A = V_M = L_{\text{eff}} \left( \frac{dX_d}{dV_{DS}} \right)^{-1} = \frac{1}{\lambda}$$

$$r_o = \frac{V_A}{I_D}$$

$$\phi_f = \frac{kT}{q} \ln \left( \frac{N_A}{n_i} \right)$$

$$\gamma = \frac{\sqrt{2q\epsilon N_A}}{C_{ox}}$$

$$V_t = V_{to} + \gamma \left( \sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right)$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

$$k' = \mu_n C_{ox}$$

$$V_{OV} = V_{GS} - V_t$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = k' \frac{W}{L} V_{OV} = \frac{2I_D}{V_{OV}}$$

$$C_{gs} = C_{gd} = \frac{C_{ox} WL}{2}$$

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}}$$

$$\frac{\partial V_t}{\partial V_{BS}} = \frac{-\gamma}{2\sqrt{2\phi_f + V_{SB}}} = -\chi$$

$$\chi = \frac{C_{js}}{C_{ox}} = \frac{g_{mb}}{g_m}$$

$$f_T = \frac{1.5\mu_n V_{OV}}{2\pi L^2}$$

$$f_T = \frac{2\mu_n}{2\pi W_B^2} V_T$$

$$I_D = I_t \frac{W}{L} \exp\left(\frac{V_{OV}}{nV_T}\right) \left[ 1 - \exp\left(\frac{-V_{DS}}{V_T}\right) \right]$$

**End of Paper**